
Sequence 110**X02122_en**

Design a sequential circuit with one binary input and one binary output. The output must be 1 at cycle i when the inputs at cycles $i-2$, $i-1$ and i are 110, otherwise the output must be 0.

Specification

```
module find110(in, out, clk, rst );
  input in, clk, rst ;
  output out;
```

Hint

The state machine can be implemented with 3 states.

Input

- clk is the clock signal
- rst is the synchronous reset signal.
- in is the binary input.

Output

- out is the output that behaves according to the specification.

Problem information

Author: Jordi Cortadella

Generation: 2026-02-03T12:22:15.110Z