

---

## **Four bit half subtractor**

**X05606\_en**

---

Create a four bit half subtractor capable of calculating the difference between two signed 4-bit numbers encoded using two's complement.

The root module must be called `sub`.

### **Input**

$x$  and  $y$  are four bit sized inputs each, encoded in two's complement.

### **Output**

$w$  is the four bit output, in two's complement ( $y - x$ )

$b$  is the 1-bit output borrow.

$ovf$  is a 1-bit signal that is raised if  $y - x$  cannot be encoded in four bits.

### **Problem information**

Author : Javier de San Pedro Martín (on behalf of Marta Miralpeix)

Generation : 2013-07-17 16:31:15

© *Jutge.org*, 2006–2013.

<http://www.jutge.org>