
Prime number

X07160_en

Design a circuit that has a 4-bit number as input. The output of the circuit must be 1 if the number represented by the input in binary code is prime, and 0 otherwise (0 and 1 are not prime).

Specification

```
module prime (n, is_prime );  
    input [3:0] n;  
    output is_prime ;
```

Input

- n is the 4-bit input number.

Output

- is_prime is the output indicating whether the number is prime or not.

Problem information

Author : Jordi Cortadella

Generation : 2013-09-02 15:56:38

© Jutge.org, 2006–2013.

<http://www.jutge.org>