

---

## Prime number

X07160\_en

---

Design a circuit that has a 4-bit number as input. The output of the circuit must be 1 if the number represented by the input in binary code is prime, and 0 otherwise (0 and 1 are not prime).

### Specification

```
module prime (n, is_prime);
  input [3:0] n;
  output is_prime;
```

### Input

- $n$  is the 4-bit input number.

### Output

- $is\_prime$  is the output indicating whether the number is prime or not.

### Problem information

Author: Jordi Cortadella

Generation: 2026-02-03T12:18:01.787Z

© Jutge.org, 2006–2026.

<https://jutge.org>