
Residue mod 7**X08834_en**

Design a circuit that computes the residue mod 7 of a 4-bit number represented in binary code.

The top module must be called *mod7*.

```
module mod7(n, residue);
    input [3:0] n;
    output [2:0] residue ;
```

Input

- *n* is a 4-bit number represented in binary code.

Output

- *residue* represents *n mod 7* in binary code.

Problem information

Author : Jordi Cortadella

Generation : 2013-07-17 16:31:56

© Jutge.org, 2006–2013.

<http://www.jutge.org>