
Sequence 110**X10202_en**

Design a sequential circuit with one binary input and one binary output. The output must be 1 at cycle i when the inputs at cycles $i - 2$, $i - 1$ and i are 110, otherwise the output must be 0.

Specification

```
module find110(in, out, clk, rst );
  input in, clk, rst ;
  output out;
```

Hint

The state machine can be implemented with 3 states.

Input

- clk is the clock signal
- rst is the synchronous reset signal.
- in is the binary input.

Output

- out is the output that behaves according to the specification.

Problem information

Author : Jordi Cortadella

Generation : 2026-01-16 13:45:24

© Jutge.org, 2006–2026.

<https://jutge.org>