
Toggle

X15508_en

A toggle is a 1-output circuit that changes state at every cycle. Design a toggle circuit that starts with the output being 0 and generates an alternating sequence of 1's and 0's, i.e., 010101010101...

Specification

```
module toggle (t, clk, rst);  
    input clk, rst;  
    output t;
```

Input

- *clk* is the clock signal.
- *rst* is the synchronous reset signal.

Output

- *t* is the output that toggles at every cycle.

Problem information

Author : Jordi Cortadella

Generation : 2013-09-02 15:58:59

© Jutge.org, 2006–2013.

<http://www.jutge.org>