
Unconventional cyclic counter

X23157_en

Design a 3-bit cyclic counter that outputs the sequence 0, 1, 3, 7, 6, 4, 0, 1, ... (of period 6).

Specification

```
module cyclic_counter(count, clk, rst );
    output [2:0] count;
    input clk, rst;
```

Input

- *clk* is the clock signal.
- *rst* is the synchronous reset signal.

Output

- *count* is the output of the counter.

Problem information

Author : Jordi Cortadella

Generation : 2013-09-02 15:57:05

© Jutge.org, 2006–2013.

<http://www.jutge.org>