
Shift left or right

X25794_en

Design a circuit that shifts an N -bus one position to the left or to the right. The direction of the shift is determined by a control signal called LR . When $LR=0$, the shift must be to the left. When $LR=1$, the shift must be to the right. N must be a parameter of the circuit with default value 8.

Specification

```
module shift_left_right (in, LR, out);  
  parameter  $N=8$ ;  
  input [ $N-1:0$ ] in;  
  input LR;  
  output [ $N-1:0$ ] out;
```

Input

- in is the N -bit input bus.
- LR is the control signal that determines the direction of the shift.

Output

- out is the value of the bus shifted one position to the left or right.

Problem information

Author: Jordi Cortadella

Generation: 2026-02-03T12:18:56.155Z

© Jutge.org, 2006–2026.

<https://jutge.org>