
Half adder

X27385_en

Design a **half adder** that is a circuit that performs the addition of two binary digits, a and b . It outputs the *sum* and the output *carry*.

Specification

```
module halfadder (a, b, sum, carry);  
    input a, b;  
    output sum, carry;
```

Input

- a and b are the two input values.

Output

- *sum* is the least significant digit of $a + b$.
- *carry* is the output carry, i.e., the most significant digit of $a + b$.

Problem information

Author : Javier de San Pedro Martín

Generation : 2025-02-09 12:09:26

© Jutge.org, 2006–2025.

<https://jutge.org>