

---

**Bus invert****X29475\_en**

Design a circuit that inverts the value of an  $N$ -bit bus.  $N$  must be a parameter of the circuit with default value 8.

**Specification**

```
module bus_invert(in, out);
    parameter N=8;
    input [N-1:0] in;
    output [N-1:0] out;
```

**Input**

- *in* is the  $N$ -bit input bus.

**Output**

- *out* is the  $N$ -bit inverted value of the bus.

**Problem information**

Author : Jordi Cortadella

Generation : 2013-09-02 15:58:31

© Jutge.org, 2006–2013.

<http://www.jutge.org>