
Add 7 bits

X31534_en

Design a circuit that receives 7 inputs and generates a 3-bit output. The output represents the number of ones at the inputs.

Specification

```
module add7bits(in, out);
    input [6:0] in;
    output [2:0] out;
```

Hint

Use only full adders.

Input

- *in* is the input vector with 7 signals.

Output

- *out* is a 3-bit number representing the number of ones at the inputs.

Problem information

Author: Jordi Cortadella

Generation: 2026-02-03T12:11:01.255Z

© Jutge.org, 2006–2026.

<https://jutge.org>