
Full adder

X31980_en

Design a **full adder**. A full adder is a circuit that performs a 1-bit addition receiving an input carry and generating an output carry.

Specification

```
module full_adder(a, b, cin, sum, cout);  
  input a, b, cin;  
  output sum, cout;
```

Input

- *a* and *b* are the two inputs.
- **cin** is the input carry.

Output

- *sum* is the sum of the two bits and the input carry.
- **cout** is the output carry.

Problem information

Author : Jordi Cortadella

Generation : 2026-01-16 13:35:14

© Jutge.org, 2006–2026.

<https://jutge.org>