
Is it a BCD digit?

X31983_en

Design a circuit that receives a 4-bit number and generates an output that indicates when the number represents a BCD digit (the value is between 0 and 9).

Specification

```
module is_bcd_digit( digit , is_bcd );  
    input [3:0] digit ;  
    output is_bcd;
```

Input

- *digit* is the 4-bit input number.

Output

- *is_bcd* indicates when the number is a BCD digit.

Problem information

Author: Jordi Cortadella

Generation: 2026-07-14T06:43:44.415Z

© *Jutge.org*, 2006–2026.

<https://jutge.org>