
Is it a BCD digit?

X31983_en

Design a circuit that receives a 4-bit number and generates an output that indicates when the number represents a BCD digit (the value is between 0 and 9).

Specification

```
module is_bcd_digit( digit , is_bcd );
    input [3:0] digit;
    output is_bcd;
```

Input

- *digit* is the 4-bit input number.

Output

- *is_bcd* indicates when the number is a BCD digit.

Problem information

Author : Jordi Cortadella

Generation : 2013-09-02 15:56:21

© Jutge.org, 2006–2013.

<http://www.jutge.org>