
4-bit counter

X35277_en

Design a circuit that implements a 4-bit counter (mod 16). The counter must start at zero after reset and increase the value at each cycle.

Specification

```
module counter4(count, clk, rst );
    input clk, rst ;
    output [3:0] count;
```

Input

- *clk* is the clock signal.
- *rst* is the synchronous reset signal.

Output

- *count* is the 4-bit output of the counter.

Problem information

Author : Jordi Cortadella

Generation : 2013-09-02 15:57:01

© Jutge.org, 2006–2013.

<http://www.jutge.org>