

---

## 4-bit ALU

## X35448\_en

---

Design a small ALU that receives two input numbers,  $a$  and  $b$ , and produces the result of an operation encoded by the signals  $op$ . There are four operations: addition ( $a + b$ , when  $op=00$ ), subtraction ( $a - b$ , when  $op=01$ ), transfer  $a$  ( $a$ , when  $op=10$ ) and double  $a$  ( $2a$ , when  $op=11$ ). The ALU also has an additional output ( $zero$ ) that is activated when the result is zero.

Design the ALU for 4-bit operands.

### Specification

```
module ALU(a, b, op, result, zero);  
  input [3:0] a, b;  
  input [1:0] op;  
  output [3:0] result;  
  output zero;
```

### Input

- $a$  and  $b$  are the two input 4-bit operands.
- $op$  indicates the type of operation.

### Output

- $result$  is the 4-bit result of the operation.
- $zero$  indicates when the result is zero.

### Problem information

Author: Jordi Cortadella

Generation: 2026-02-03T12:14:10.513Z