

---

## Even number

X36253\_en

---

Design a circuit that receives a 4-bit number as input and produces an output that is asserted when the input number is even.

### Specification

```
module even4(number, even);
    input [3:0] number;
    output even;
```

### Input

- *number* is the 4-bit input number.

### Output

- *even* indicates when the input number is even.

### Problem information

Author: Jordi Cortadella

Generation: 2026-02-03T12:15:09.029Z

© Jutge.org, 2006–2026.

<https://jutge.org>