
n-bit comparator**X37457_en**

Design a circuit that compares two n -bit numbers represented in binary code and indicates whether the first is greater than, equal to or smaller than the second.

The number of bits of the numbers must be a parameter of the module with a default value as shown in the specification.

Specification

```
module cmp(a, b, eq, gt, lt);
  parameter N=16;
  input [N-1:0] a, b;
  output eq, gt, lt;
```

Hint

Design a 1-bit comparator that receives the result of the comparison of the least-significant bits. Use n instances of this circuit.

Input

- a and b are the two n -bit input numbers.

Output

- eq indicates that $a=b$.
- gt indicates that $a>b$.
- lt indicates that $a<b$.

Problem information

Author: Jordi Cortadella

Generation: 2026-02-03T12:12:42.691Z

© Jutge.org, 2006–2026.

<https://jutge.org>