
n-bit comparator

X37457_en

Design a circuit that compares two *n*-bit numbers represented in binary code and indicates whether the first is greater than, equal to or smaller than the second.

The number of bits of the numbers must be a parameter of the module with a default value as shown in the specification.

Specification

```
module cmp(a, b, eq, gt, lt);
    parameter N=16;
    input [N-1:0] a, b;
    output eq, gt, lt;
```

Hint

Design a 1-bit comparator that receives the result of the comparison of the least-significant bits. Use *n* instances of this circuit.

Input

- *a* and *b* are the two *n*-bit input numbers.

Output

- *eq* indicates that $a=b$.
- *gt* indicates that $a>b$.
- *lt* indicates that $a<b$.

Problem information

Author : Jordi Cortadella

Generation : 2013-09-02 15:58:49

© Jutge.org, 2006–2013.

<http://www.jutge.org>