

---

## Max of two numbers

X37473\_en

---

Design a circuit receives two 3-bit numbers at the input and produces the maximum of both numbers at the output.

### Specification

```
module max3(a, b, max);  
    input [2:0] a, b;  
    output [2:0] max;
```

### Input

- $a$  and  $b$  are the two 3-bit input numbers.

### Output

- $max$  is the 3-bit output number.

### Problem information

Author : Jordi Cortadella

Generation : 2013-09-02 15:56:30

© Jutge.org, 2006–2013.

<http://www.jutge.org>