
4-bit adder/subtractor

X42916_en

Design a circuit that performs the addition or subtraction of two 4-bit numbers. The result (mod 16) must be represented in 4 bits also. The circuit has an input (*op*) that indicates which operation must be performed (0 for addition, 1 for subtraction).

Specification

```
module add_sub4(a, b, op, result );
  input [3:0] a, b;
  input op;
  output [3:0] result ;
```

Input

- *a* and *b* are the two 4-bit operands.
- *op* indicates the type of operation (0 for addition, 1 for subtraction).

Output

- *result* is the 4-bit result of the operation (mod 16).

Problem information

Author: Jordi Cortadella

Generation: 2026-02-03T12:11:46.582Z

© Jutge.org, 2006–2026.
<https://jutge.org>