

---

## Mod-7 up-down counter

X56911\_en

---

Design a mod-7 up-down counter. The counter must *count-up* when the input signal *up* is 1. Otherwise, the counter must *count-down*. After reset, the counter must be initialized at zero.

### Specification

```
module updown_mod7(up, count, clk, rst);
    input up, clk, rst;
    output [2:0] count;
```

### Input

- *up* is the input signal that indicates when the counter must count-up (1) or count-down (0).
- *clk* is the clock signal.
- *rst* is the synchronous reset signal.

### Output

- *count* is the 3-bit output.

### Problem information

Author : Jordi Cortadella

Generation : 2013-09-02 15:57:29

© Jutge.org, 2006–2013.

<http://www.jutge.org>