
4-bit incrementer

X58456_en

Design a circuit that receives a 4-bit number and produces the same number increased by one unit (mod 16).

Specification

```
module incr4(in, out);  
    input [3:0] in;  
    output [3:0] out;
```

Input

- *in* represents the 4-bit input number.

Output

- *out* represents the 4-bit output number.

Problem information

Author: Jordi Cortadella

Generation: 2026-02-03T12:13:24.463Z

© *Jutge.org*, 2006–2026.

<https://jutge.org>