
Recognizing sequences

X60084_en

Design a sequential circuit with one binary input and one binary output. The output at time t is 1 when the input in the time interval $[t - 3, t]$ is 0101 or 0110.

Specification

```
module sequence(in, out, clk, rst );  
    input in, clk, rst ;  
    output out;
```

Hint

The state machine can be implemented with 5 states.

Input

- in is the input of the state machine.
- clk is the clock signal.
- rst is the synchronous reset signal.

Output

- out is the output of the state machine.

Problem information

Author : Jordi Cortadella

Generation : 2013-09-02 15:57:25

© Jutge.org, 2006–2013.

<http://www.jutge.org>