
1-bit comparator

X60848_en

Design a circuit that compares two bits and indicates whether the first is greater than, equal to or smaller than the second.

The top module must be called *cmp*.

```
module cmp(a, b, eq, gt, lt );
    input a, b;
    output eq, gt, lt;
```

Input

- *a* and *b* are the input bits

Output

- *eq* indicates that $a=b$.
- *gt* indicates that $a>b$.
- *lt* indicates that $a<b$.

Problem information

Author : Jordi Cortadella

Generation : 2013-07-17 16:31:38

© Jutge.org, 2006–2013.

<http://www.jutge.org>