
Two or more ones**X67345_en**

Design a circuit that receives four inputs and produces one output. The output must be 1 when there are two or more inputs at 1. Otherwise, the output must be 0.

Specification

```
module two_or_more_ones(a, b, c, d, out);
    input a, b, c, d;
    output out;
```

Input

- a, b, c and d are the four inputs.

Output

- out is the output.

Problem information

Author : Jordi Cortadella

Generation : 2013-09-02 15:56:26

© Jutge.org, 2006–2013.

<http://www.jutge.org>