
Majority of 5 inputs

X72286_en

Design a circuit that implements the 5-input majority function, that is, the output is 1 when there are more ones than zeros at the inputs.

Specification

```
module majority(a, b, c, d, e, maj);  
    input a, b, c, d, e;  
    output maj;
```

Input

- a, b, c, d and e are the inputs.

Output

- maj is the output implementing the majority function.

Problem information

Author : Jordi Cortadella

Generation : 2013-09-02 15:56:28

© Jutge.org, 2006–2013.

<http://www.jutge.org>