

---

## Vending machine


X77254\_en

---

We have to design the control of a vending machine that dispenses a bag of cookies for 3€. The machine only accepts 1€ and 2€ coins. The machine has a coin slot that detects the insertion of a coin and distinguishes between 1€ and 2€ coins. Each time a coin is inserted, a 1-cycle pulse is generated on signal *E1* or *E2*, depending on the type of coin. Since the machine only has one coin slot, no two coins can be inserted simultaneously.

After the insertion of 3€, the machine must dispense a bag of cookies by activating a signal called *Cookies* for one cycle. Additionally, if the customer has inserted 4€, the machine will dispense a 1€ change by activating the signal *Change* on the same cycle the cookies are dispensed.

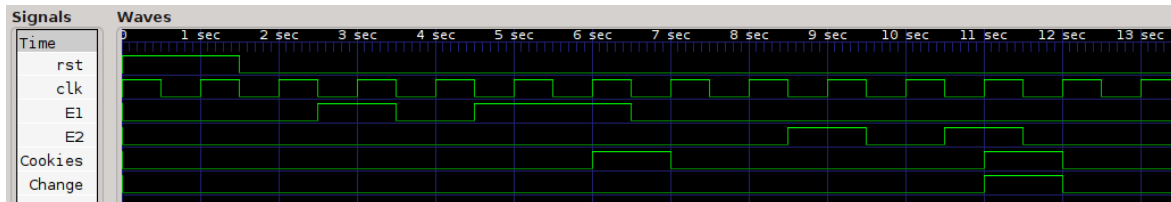The machine will not accept more coins while the cookies and the change are dispensed. The following figure illustrates a possible waveform of the vending machine control.



### Specification

```
module Vending_Machine(E1, E2, Cookies, Change, clk, rst );
    input E1, E2, clk, rst ;
    output Cookies, Change;
```

### Hint

The state machine can be implemented with 5 states.

### Input

- *E1* is the input indicating the insertion of a 1€ coin.
- *E2* is the input indicating the insertion of a 2€ coin.
- *clk* is the clock signal.
- *rst* is the synchronous reset signal.

### Output

- *Cookies* is the output that activates the delivery of cookies.
- *Change* is the output that activates the return of change.

**Problem information**

Author : Jordi Cortadella

Generation : 2013-09-02 15:57:32

© *Jutge.org*, 2006–2013.

<http://www.jutge.org>