
Two or more ones**X78683_en**

Design a circuit that receives four inputs and produces one output. The output must be 1 when there are two or more inputs at 1. Otherwise, the output must be zero.

The top module must be called *two_or_more_ones*.

```
module two_or_more_ones(a, b, c, d, out);
    input a, b, c, d;
    output out;
```

Input

- *a, b, c* and *d* are the four inputs.

Output

- *out* is the output.

Problem information

Author : Jordi Cortadella

Generation : 2013-07-17 16:31:34

© Jutge.org, 2006–2013.

<http://www.jutge.org>