

---

## 2-bit counter

## X81362\_en

---

Design a 2-bit counter. The counter starts at zero and increments once at every rising edge when input *inc* is 1. If *rst* is active during a rising edge, the clock goes back to 0, ignoring *inc* for that cycle.

### Specification

```
module counter(clk, rst, inc, count);
    input clk, rst;
    input inc;
    output [1:0] count;
```

### Input

- *clk* is the clock signal.
- *rst* is the synchronous reset signal.
- *inc* is the *increment* signal.

### Output

- *count* is the 2-bit output.

### Problem information

Author: Javier de San Pedro Martín

Generation: 2026-02-03T12:20:36.726Z

© Jutge.org, 2006–2026.

<https://jutge.org>