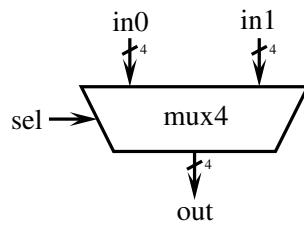

2-input multiplexer with 4-bit signals**X82780_en**

Design a 2-input multiplexer in which the inputs are 4-bit wide. The selection signal is called *sel*, whereas the two inputs are called *in0* and *in1*. The output will be *in0* when *sel*=0 and *in1* when *sel*=1.

**Specification**

```
module mux4(in0, in1, sel, out);
  input [3:0] in0, in1;
  input sel;
  output [3:0] out;
```

Input

- *in0* and *in1* are the two 4-bit inputs.
- *sel* is the selector.

Output

- *out* is the 4-bit output.

Problem information

Author: Javier de San Pedro Martín and Marta Miralpeix Anglerill

Generation: 2026-02-03T12:17:09.360Z

© Jutge.org, 2006–2026.

<https://jutge.org>