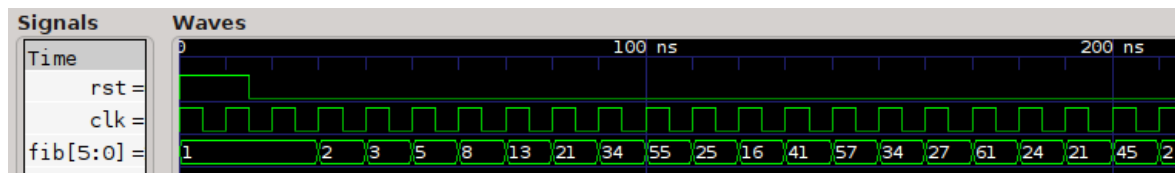


Fibonacci

X95484_en

Design a sequential circuit that generates the Fibonacci series. The circuit will represent the numbers with n bits and will generate the Fibonacci numbers $\text{mod } 2^n$. At each cycle, a new number must be generated. The following waveform illustrates the behavior of the circuit.



The circuit must be designed to represent the numbers with 6 bits.

Specification

```
module fibonacci(clk, rst, fib);  
    input clk, rst;  
    output [5:0] fib;
```

Input

- *clk* is the clock signal.
- *rst* is the synchronous reset signal.

Output

- *fib* is the Fibonacci number generated at each cycle.

Problem information

Author : Jordi Cortadella

Generation : 2013-09-02 15:58:14

© Jutge.org, 2006–2013.

<http://www.jutge.org>